

Electronic Devices

Ninth Edition
Floyd

Chapter 4: Bipolar Junction Transistors

Summary

BJT Structure

The BJT has three regions called the emitter, base, and collector. Between the regions are junctions as indicated.

The base is a thin lightly doped region compared to the heavily doped emitter and moderately doped collector regions.

© 2012 Pearson Education, Upper Saddle River, NJ, 07458. All rights reserved.

Summary

BJT Operation

In normal operation, the base-emitter is forward-biased and the base-collector is reverse-biased.

For the *npn* type shown, the collector is more positive than the base, which is more positive than the emitter.

For the *pnp* type, the voltages are reversed to maintain the forward-reverse bias.

© 2012 Pearson Education, Upper Saddle River, NJ, 07458. All rights reserved.

Summary

BJT Currents

The direction of conventional current is the direction of the arrow on the emitter terminal. The emitter current is the sum of the collector current and the small base current. That is, $I_E = I_C + I_B$.

© 2012 Pearson Education, Upper Saddle River, NJ, 07458. All rights reserved.

Summary

BJT Characteristics

The collector characteristic curves show the relationship of the three transistor currents.

The curve shown is for a fixed based current. The first region is the **saturation region**.

As V_{CE} is increased, I_C increases until *B*. Then it flattens in region between points *B* and *C*, which is the **active region**.

After *C*, is the **breakdown region**.

© 2012 Pearson Education, Upper Saddle River, NJ, 07458. All rights reserved.

Summary

BJT Characteristics

The collector characteristic curves illustrate the relationship of the three transistor currents.

By setting up other values of base current, a family of collector curves is developed.

β_{DC} is the ratio of collector current to base current.

$$\beta_{DC} = \frac{I_C}{I_B}$$

It can be read from the curves. The value of β_{DC} is nearly the same wherever it is read.

© 2012 Pearson Education, Upper Saddle River, NJ, 07458. All rights reserved.

Summary

BJT Characteristics

Example: What is the β_{DC} for the transistor shown?

Solution:
 Choose a base current near the center of the range – in this case I_{B3} which is $30 \mu\text{A}$.
 Read the corresponding collector current – in this case, 5.0 mA . Calculate the ratio:

$$\beta_{DC} = \frac{I_C}{I_B} = \frac{5.0 \text{ mA}}{30 \mu\text{A}} = 167$$

© 2012 Pearson Education, Upper Saddle River, NJ, 07458. All rights reserved.

Summary

Cutoff

In a BJT, **cutoff** is the condition in which there is no base current, which results in only an extremely small leakage current (I_{CEO}) in the collector circuit. For practical work, this current is assumed to be zero.

In cutoff, neither the base-emitter junction, nor the base-collector junction are forward-biased.

© 2012 Pearson Education, Upper Saddle River, NJ, 07458. All rights reserved.

Summary

Saturation

In a BJT, **saturation** is the condition in which there is maximum collector current. The saturation current is determined by the external circuit (V_{CC} and R_C in this case) because the collector-emitter voltage is minimum ($\approx 0.2 \text{ V}$)

In saturation, an increase of base current has no effect on the collector circuit and the relation $I_C = \beta_{DC} I_B$ is no longer valid.

© 2012 Pearson Education, Upper Saddle River, NJ, 07458. All rights reserved.

Summary

DC Load Line

The **DC load line** represents the circuit that is external to the transistor. It is drawn by connecting the saturation and cutoff points.

The transistor characteristic curves are shown superimposed on the load line. The region between the saturation and cutoff points is called the **active region**.

© 2012 Pearson Education, Upper Saddle River, NJ, 07458. All rights reserved.

Summary

DC Load Line

Example: What is the saturation current and the cutoff voltage for the circuit? Assume $V_{CE} = 0.2 \text{ V}$ in saturation.

Solution:

$$I_{SAT} = \frac{V_{CC} - 0.2 \text{ V}}{R_C} = \frac{15 \text{ V} - 0.2 \text{ V}}{3.3 \text{ k}\Omega} = 4.48 \text{ mA} \quad V_{CO} = V_{CC} = 15 \text{ V}$$

Follow-up:
 Is the transistor saturated? $I_B = \frac{3.0 \text{ V} - 0.7 \text{ V}}{220 \text{ k}\Omega} = 10.45 \mu\text{A}$
 $I_C = \beta I_B = 200 (10.45 \mu\text{A}) = 2.09 \text{ mA}$ Since $I_C < I_{SAT}$, it is not saturated.

© 2012 Pearson Education, Upper Saddle River, NJ, 07458. All rights reserved.

Summary

Data Sheets

Data sheets give manufacturer's specifications for maximum operating conditions, thermal, and electrical characteristics. For example, an electrical characteristic is β_{DC} , which is given as h_{FE} . The 2N3904 shows a range of β 's on the data sheet from 100 to 300 for $I_C = 10 \text{ mA}$.

Characteristic	Symbol	Min	Max	Unit
ON Characteristics				
DC current gain				
($I_C = 0.1 \text{ mA dc}$, $V_{CE} = 1.0 \text{ V dc}$)	2N3903	40	—	
	2N3904	40	—	
($I_C = 1.0 \text{ mA dc}$, $V_{CE} = 1.0 \text{ V dc}$)	2N3903	35	—	
	2N3904	70	—	
($I_C = 10 \text{ mA dc}$, $V_{CE} = 1.0 \text{ V dc}$)	2N3903	50	150	
	2N3904	100	300	
($I_C = 50 \text{ mA dc}$, $V_{CE} = 1.0 \text{ V dc}$)	2N3903	30	—	
	2N3904	60	—	
($I_C = 100 \text{ mA dc}$, $V_{CE} = 1.0 \text{ V dc}$)	2N3903	15	—	
	2N3904	30	—	

© 2012 Pearson Education, Upper Saddle River, NJ, 07458. All rights reserved.

Summary

DC and AC Quantities

The text uses capital letters for both AC and DC currents and voltages with rms values assumed unless stated otherwise.

DC Quantities use upper case roman subscripts. Example: V_{CE} . (The second letter in the subscript indicates the reference point.)

AC Quantities and time varying signals use lower case italic subscripts. Example: V_{ce} .

Internal transistor resistances are indicated as lower case quantities with a prime and an appropriate subscript. Example: $r_{e'}$.

External resistances are indicated as capital R with either a capital or lower case subscript depending on if it is a DC or ac resistance. Examples: R_C and R_c .

Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Summary

BJT Amplifiers

A BJT amplifies AC signals by converting some of the DC power from the power supplies to AC signal power. An ac signal at the input is superimposed in the dc bias by the capacitive coupling. The output ac signal is inverted and rides on a dc level of V_{CE} .

Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Summary

BJT Switches

A BJT can be used as a switching device in logic circuits to turn on or off current to a load. As a switch, the transistor is normally in either cutoff (load is OFF) or saturation (load is ON).

In cutoff, the transistor looks like an open switch.

In saturation, the transistor looks like a closed switch.

Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Summary

Phototransistors

A phototransistor produces base current when light strikes the exposed photosensitive base region, which is the active area. Phototransistors have high gain and are more sensitive to light than photodiodes.

In a typical circuit the base lead is left open. In the circuit shown, the output voltage is maximum with no light and drops with increasing light.

Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Summary

Phototransistors

The characteristic curves for a phototransistor are based on light flux (mW/cm^2) to the base rather than base current in an ordinary transistor.

Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Summary

Phototransistors

The output from the phototransistor can be used to activate or deactivate a relay. In this case, the phototransistor is part of a switching circuit.

Question:
Is either transistor ON for the circuit when there is no incident light?


Answer:
With no incident light, Q_1 will be biased OFF. Q_2 will be forward-biased through R and is ON. Collector current in Q_2 causes the relay to be energized.

Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Summary

Optocouplers

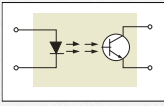An optocoupler is a single package containing an LED and a phototransistor. Optical couplers transfer a signal from one circuit to another while providing a high degree of isolation.




A key specification for optocouplers is the current transfer ratio or CTR, which is a measure of efficiency. The CTR is the ratio of output current to input current. Typically values are from 50% to 110% for standard optocouplers.

Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.


Summary

Applications for Optocouplers

Optocouplers are used when data or signals need to be transferred from a control circuit to a power circuit without making electrical connections between the circuits. For example, the logic circuits in a traffic light controller need to be isolated from the lights themselves.



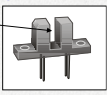Another application for optocouplers is as a transducer to detect a light path such as a hole in a rotating disk. In this case, the LED and phototransistor are separated by a gap.




Optocouplers are also useful for isolating patients from the monitoring instruments.

Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Summary

A Sample of Common Transistor Packages

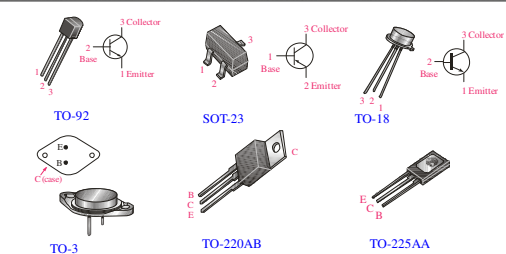


Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Summary

BJT Basic Test

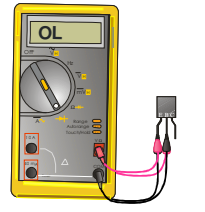A basic test for a BJT is to use the **Diode Test** function of your DMM.



To test the base-emitter junction of a BJT, connect the positive lead to the base and the negative lead to the emitter. You should see a voltage close to 0.7 V for an *npn* transistor.

Reversing the leads will show OL for "overload".

The procedure is repeated to test the base-collector junction.

Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Selected Key Terms

BJT (bipolar junction transistor) a transistor constructed with three doped semiconductor regions separated by two *pn* junctions.

Emitter the most heavily doped of the three semiconductor regions of a BJT.

Base one of the three semiconductor regions of a BJT. The base is thin and lightly doped compared to the other regions.

Collector the largest of the three semiconductor regions of a BJT.

Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Selected Key Terms

Beta the ratio of dc collector current to the dc base current in a BJT; current gain from base to collector.

Saturation the state of a BJT in which the collector current has reached a maximum and is independent of the base current.

Cutoff the nonconducting state of a transistor.

Phototransistor a transistor in which base current is produced when light strikes the photosensitive semiconductor base region.

Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Quiz

1. The region on the characteristic curve in which the current changes only slightly with an increase in V_{CE} is called the

- saturation region
- cutoff region
- breakdown region
- active region

Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Quiz

2. β_{DC} is defined as the ratio of

- collector current to base current
- collector current to emitter current
- emitter current to base current
- emitter current to collector current

Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Quiz

3. When a BJT is in saturation, the

- collector current does not change with an increase in base current
- base current cannot increase
- collector to emitter voltage is maximum
- all of the above

Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Quiz

4. When a BJT is cutoff, the

- voltage from collector to emitter is near zero
- collector current is near zero
- base-emitter junction is forward-biased
- none of the above

Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Quiz

5. The lower end of the dc load line touches the x -axis at


- saturation
- cutoff
- breakdown
- 0.7 V

Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Quiz

6. For the circuit shown, the base current is

- 1.0 μA
- 1.16 μA
- 10 μA
- 11.6 μA

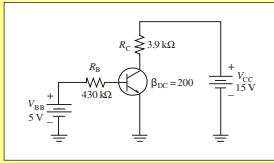

Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Quiz

7. For the circuit shown, the saturation current is

- 200 μ A
- 2.0 mA
- 3.79 mA
- 14.8 mA

Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Quiz

8. For the phototransistor circuit, assume there is sufficient light to saturate Q_1 . In this condition,

- Q_2 is also saturated
- the diode is conducting
- the relay is energized
- none of the above

Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Quiz

9. An optocoupler is a single package containing

- two transistors
- an LED and a phototransistor
- a phototransistor and a relay
- an LED and a relay

Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Quiz

10. The transistor package that is a TO-3 case is

-
-
-
-

Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Quiz

Answers:

1. d	6. c
2. a	7. c
3. a	8. d
4. d	9. b
5. b	10. c

Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.