

Summary

Voltage-Divider Bias

Now write KVL around the base emitter circuit and solve for I_E .

$$V_{TH} = I_B R_{TH} + V_{BE} + I_E R_E$$

$$I_E = \frac{V_{TH} - V_{BE}}{R_E + R_{TH} / \beta_{DC}}$$

Substituting and solving,

$$I_E = \frac{4.62 \text{ V} - 0.7 \text{ V}}{680 \Omega + 8.31 \text{ k}\Omega / 200} = 5.43 \text{ mA}$$

and $V_E = I_E R_E = (5.43 \text{ mA})(0.68 \text{ k}\Omega) = 3.69 \text{ V}$

© 2012 Pearson Education, Upper Saddle River, NJ, 07458. All rights reserved.

Summary

Voltage-Divider Bias

Multisim allows you to do a quick check of your result.

© 2012 Pearson Education, Upper Saddle River, NJ, 07458. All rights reserved.

Summary

Voltage-Divider Bias

A *pnp* transistor can be biased from either a positive or negative supply. Notice that (b) and (c) are the same circuit; both with a positive supply.

© 2012 Pearson Education, Upper Saddle River, NJ, 07458. All rights reserved.

Summary

Voltage-Divider Bias

Example: Determine I_E for the *pnp* circuit. Assume a stiff voltage divider (no loading effect).

Solution:

$$V_B = \left(\frac{R_1}{R_1 + R_2} \right) V_{EE} = \left(\frac{27 \text{ k}\Omega}{27 \text{ k}\Omega + 12 \text{ k}\Omega} \right) (+15.0 \text{ V}) = 10.4 \text{ V}$$

$$V_E = V_B + V_{BE} = 10.4 \text{ V} + 0.7 \text{ V} = 11.1 \text{ V}$$

$$I_E = \frac{V_{EE} - V_E}{R_E} = \frac{15.0 \text{ V} - 11.1 \text{ V}}{680 \Omega} = 5.74 \text{ mA}$$

© 2012 Pearson Education, Upper Saddle River, NJ, 07458. All rights reserved.

Summary

Emitter Bias

Emitter bias has excellent stability but requires both a positive and a negative source.

For troubleshooting analysis, assume that V_E for an *npn* transistor is about -1 V .

Example: Assuming that V_E is -1 V , what is I_E ?

Solution:

$$I_E = \frac{-V_{EE} - V_E}{R_E} = \frac{-15 \text{ V} - (-1 \text{ V})}{7.5 \text{ k}\Omega} = -1.87 \text{ mA}$$

© 2012 Pearson Education, Upper Saddle River, NJ, 07458. All rights reserved.

Summary

Emitter Bias

A check with Multisim shows that the assumption for troubleshooting purposes is reasonable.

For detailed analysis work, you can include the effect of β_{DC} . In this case,

$$I_E = \frac{-V_{EE} - V_E}{R_E + R_B / \beta_{DC}}$$

© 2012 Pearson Education, Upper Saddle River, NJ, 07458. All rights reserved.


Summary

Base Bias

Base bias is used in switching circuits because of its simplicity, but not widely used in linear applications because the *Q*-point is β dependent. Base current is derived from the collector supply through a large base resistor.

Example: What is I_B ?

Solution:
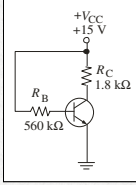
$$I_B = \frac{V_{CC} - 0.7\text{ V}}{R_B} = \frac{15\text{ V} - 0.7\text{ V}}{560\text{ k}\Omega} = 25.5\ \mu\text{A}$$


Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Summary

Base Bias


Follow up: Compare V_{CE} for the case where $\beta = 100$ and $\beta = 200$.

Solution:

For $\beta = 100$: $I_C = \beta I_B = (100)(25.5\ \mu\text{A}) = 2.55\text{ mA}$

$$V_{CE} = V_{CC} - I_C R_C = 15\text{ V} - (2.55\text{ mA})(1.8\text{ k}\Omega) = 10.4\text{ V}$$

For $\beta = 300$: $I_C = \beta I_B = (300)(25.5\ \mu\text{A}) = 7.65\text{ mA}$
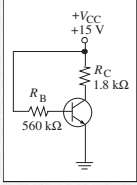
$$V_{CE} = V_{CC} - I_C R_C = 15\text{ V} - (7.65\text{ mA})(1.8\text{ k}\Omega) = 1.23\text{ V}$$


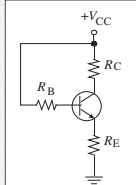
Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Summary

Emitter-Feedback Bias

An emitter resistor changes base bias into emitter-feedback bias, which is more predictable. The emitter resistor is a form of **negative feedback**.

The equation for emitter current is found by writing KVL around the base circuit. The result is:

$$I_E = \frac{V_{CC} - V_{BE}}{R_E + R_B / \beta_{DC}}$$


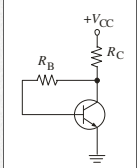
Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Summary

Collector-Feedback Bias

Collector feedback bias uses another form of **negative feedback** to increase stability. Instead of returning the base resistor to V_{CC} , it is returned to the collector.

The equation for collector current is found by writing KVL around the base circuit. The result is

$$I_C = \frac{V_{CC} - V_{BE}}{R_C + R_B / \beta_{DC}}$$


Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Summary

Collector-Feedback Bias


Example: Compare I_C for the case when $\beta = 100$ with the case when $\beta = 300$.

Solution:

When $\beta = 100$,

$$I_C = \frac{V_{CC} - V_{BE}}{R_C + R_B / \beta_{DC}} = \frac{15\text{ V} - 0.7\text{ V}}{1.8\text{ k}\Omega + 330\text{ k}\Omega / 100} = 2.80\text{ mA}$$

When $\beta = 300$,
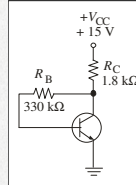
$$I_C = \frac{V_{CC} - V_{BE}}{R_C + R_B / \beta_{DC}} = \frac{15\text{ V} - 0.7\text{ V}}{1.8\text{ k}\Omega + 330\text{ k}\Omega / 300} = 4.93\text{ mA}$$


Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Key Terms

- Q-point** The dc operating (bias) point of an amplifier specified by voltage and current values.
- DC load line** A straight line plot of I_C and V_{CE} for a transistor circuit.
- Linear region** The region of operation along the load line between saturation and cutoff.
- Stiff voltage divider** A voltage divider for which loading effects can be ignored.
- Feedback** The process of returning a portion of a circuit's output back to the input in such a way as to oppose or aid a change in the output.

Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Quiz

1. A signal that swings outside the active area will be

- clamped
- clipped
- unstable
- all of the above

© 2012 Pearson Education, Upper Saddle River, NJ, 07458. All rights reserved.

Quiz

2. A stiff voltage divider is one in which


- there is no load current
- divider current is small compared to load current
- the load is connected directly to the source voltage
- loading effects can be ignored

© 2012 Pearson Education, Upper Saddle River, NJ, 07458. All rights reserved.

Quiz

3. Assuming a stiff voltage-divider for the circuit shown, the emitter voltage is

- 4.3 V
- 5.7 V
- 6.8 V
- 9.3 V

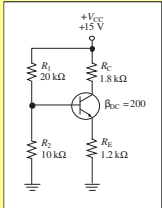


© 2012 Pearson Education, Upper Saddle River, NJ, 07458. All rights reserved.

Quiz

4. For the circuit shown, the dc load line will intersect the y-axis at

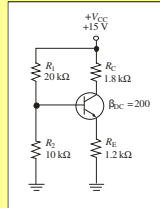- 5.0 mA
- 10.0 mA
- 15.0 mA
- none of the above




© 2012 Pearson Education, Upper Saddle River, NJ, 07458. All rights reserved.

Quiz

5. If you Thevenize the input voltage divider, the Thevenin resistance is

- 5.0 kΩ
- 6.67 kΩ
- 10 kΩ
- 30 kΩ

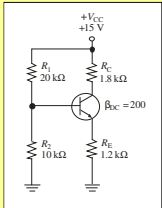


© 2012 Pearson Education, Upper Saddle River, NJ, 07458. All rights reserved.

Quiz

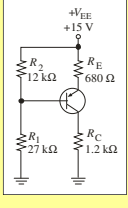6. For the circuit shown, the emitter voltage is

- less than the base voltage
- less than the collector voltage
- both of the above
- none of the above



© 2012 Pearson Education, Upper Saddle River, NJ, 07458. All rights reserved.

Quiz

7. Emitter bias


- a. is not good for linear circuits
- b. uses a voltage-divider on the input
- c. requires dual power supplies
- d. all of the above

Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Quiz

8. With the emitter bias shown, a reasonable assumption for troubleshooting work is that the

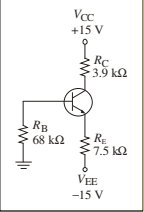- a. base voltage = +1 V
- b. emitter voltage = +5 V
- c. emitter voltage = -1 V
- d. collector voltage = V_{CC}




Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Quiz

9. The circuit shown is an example of

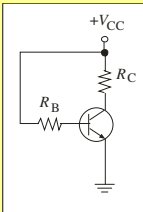- a. base bias
- b. collector-feedback bias
- c. emitter bias
- d. voltage-divider bias




Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Quiz

10. The circuit shown is an example of

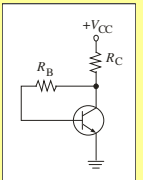- a. base bias
- b. collector-feedback bias
- c. emitter bias
- d. voltage-divider bias



Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.

Quiz

Answers:

1. b	6. d
2. d	7. c
3. a	8. c
4. a	9. a
5. b	10. b

Electronic Devices, 9th edition
Thomas L. Floyd
© 2012 Pearson Education, Upper Saddle River, NJ, 07458.
All rights reserved.